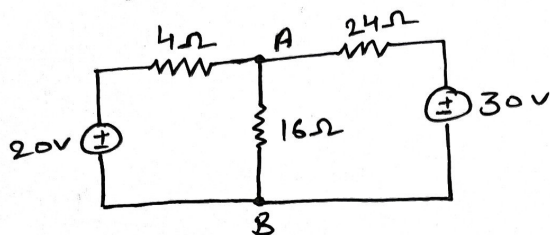


LAKSHAY MALIK
131220030045

Assignment 1 [Electrical Science]

Ques 1 Find Thevenin Equivalent Circuit and Norton Equivalent Circuit.




Ans:

Thevenin

Load Resistance $R_L = 16\ \Omega$

Step 1: Remove R_L and calculate V_{Th}

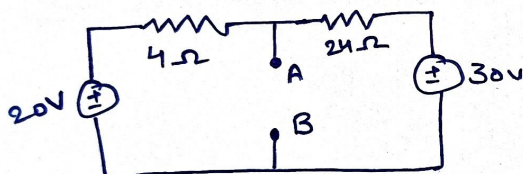

$$I = \frac{V}{R} = \frac{30 - 20}{24 + 4} = \frac{10}{28}$$


$$I = 0.357\text{ A}$$

Voltage Drop [V_{Th}]

$$V_{Th} = 30 - [24 \times 0.357]$$

$$V_{Th} = 21.4\text{ V}$$

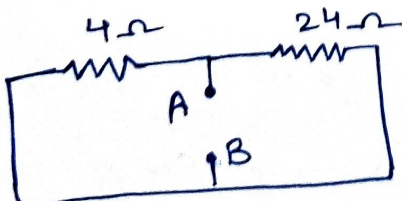
Step 2: Remove R_L and replace all active sources with their internal resistances



Norton

Load Resistance $R_L = 16\ \Omega$

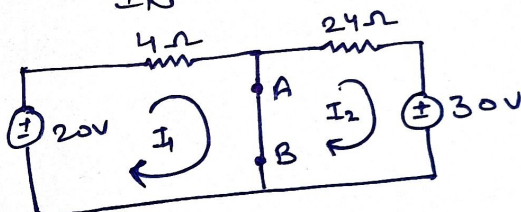Step 1: Replace R_L with short circuit branch and calculate I_N



Applying KVL in Mesh 1

$$20 - 4I_1 = 0$$

$$I_1 = 5\text{ A}$$

Applying KVL in Mesh 2


$$-30 - 24I_2 = 0$$

$$I_2 = -1.25\text{ A}$$

$$I_N = I_1 - I_2 = 5 - (-1.25)$$

$$I_N = 6.25\text{ A}$$

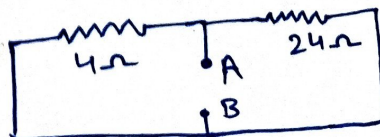Step 2: Remove R_L and replace all active sources with their internal resistances




Step 3 : Calculate R_{th}

$$R_{th} = \frac{4 \times 24}{4 + 24}$$

$$R_{th} = 3.428 \Omega$$

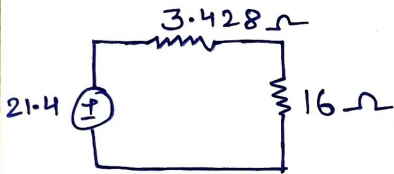Step 4 : Draw Thevenin's Equivalent Circuit




Step 3: Calculate R_N


$$R_N = \frac{4 \times 24}{4 + 24}$$

$$R_N = 3.428 \Omega$$

Step 4 : Draw Norton's Equivalent Circuit

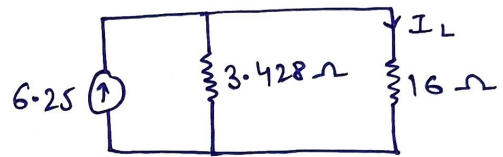

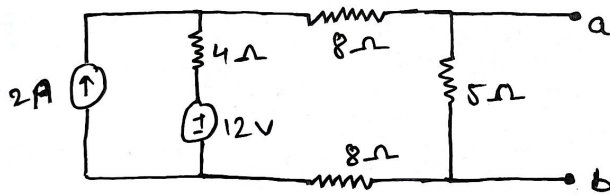
Ques 2 : Find the Norton equivalent circuit at terminals a-b of the electrical circuit given below.




Ans: Step 1: Identify Load Terminals

Load Terminal: a-b

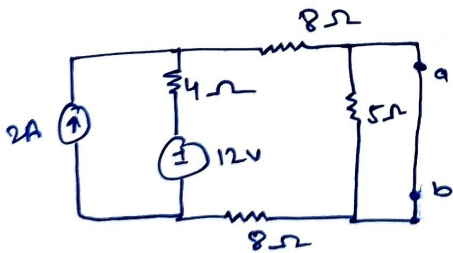Step 2: Replace R_L with short circuit branch and calculate I_N



5 Ω will be short circuited \Rightarrow

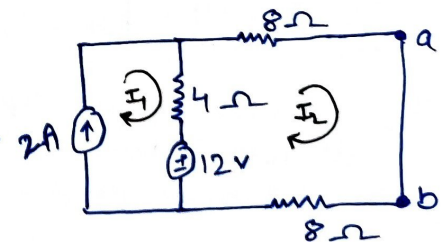

Apply KVL in Mesh ①

$$I_1 = 2A$$

Apply KVL in Mesh ②

$$12 - (4(I_2 - I_1)) - 8I_2 - 8I_2 = 0$$

$$12 - 20I_2 + 4I_1 = 0$$


$$-20I_2 = -20$$

$$I_2 = 1A$$

$$I_N = I_2 = 1A$$

$$I_N = 1A$$

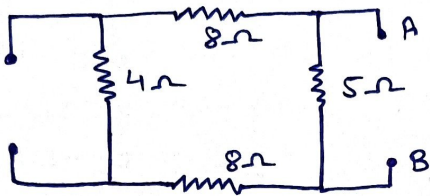step 3: Remove R_L and replace all active sources with their internal resistances.




step 4: Calculate R_N

$$R_N = (8+8+4) \parallel 5$$


$$= \frac{20 \times 5}{20+5} = 4$$

$$R_N = 4\Omega$$

step 5: Draw Norton's Equivalent Circuit

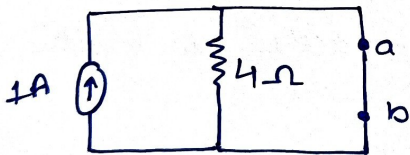

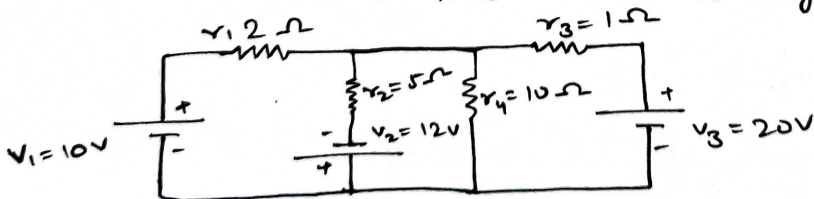
Ques 3: Find the current through the 10 ohm resistor using Thevenin's ~~Resis~~ Theorem in circuit given below.



ans: step 1: Identify Load Resistance

$$R_L = 10\Omega$$

step 2: Remove R_L and calculate V_{th}

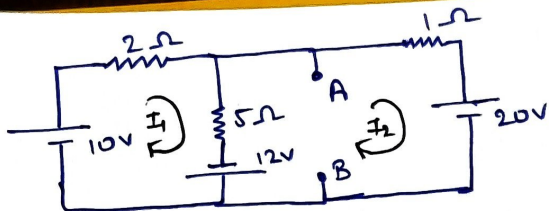

apply KVL in Mesh ①

$$12 + 10 - 2I_1 - 5(I_1 - I_2) = 0$$

$$22 - 2I_1 - 5I_1 + 5I_2 = 0$$

$$22 - 7I_1 + 5I_2 = 0$$

$$\boxed{7I_1 - 5I_2 = 22} \quad \text{--- ①}$$

apply KVL in Mesh ②

$$-20 - 12 - 5(I_2 - I_1) - 1I_2 = 0$$

$$-22 - 5I_2 + 5I_1 - I_2 = 0$$

$$-22 - 6I_2 + 5I_1 = 0$$

$$\boxed{5I_1 - 6I_2 = 22} \quad \text{--- ②}$$

From ① & ②


$$\boxed{I_1 = -1.64 \text{ A}}$$

$$\boxed{I_2 = -6.70 \text{ A}}$$

Voltage Drop = $20 + (-6.70 \times 1)$
 $= 13.3$

$$\boxed{V_{Th} = 13.3 \text{ V}}$$

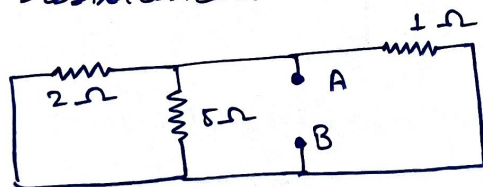Step 3: Remove R_L and replace all active sources with their internal resistances.



Step 4: Calculate R_{Th}


$$R_{Th} = R_{eq}$$

$$\frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{5} + \frac{1}{10} = \frac{5+2+1}{5 \times 2}$$

$$R_{eq} = \frac{10}{17} \Omega$$

$$\boxed{R_{Th} = \frac{10}{17} \Omega}$$

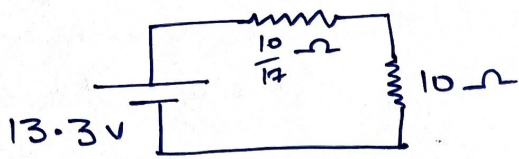
step 5: Draw Thevenin's Equivalent circuit




$$I_L = \frac{13.3}{\frac{10}{17} + 10} = 1.25 \text{ A}$$

Current through 10 ohm resistor = 1.25 A

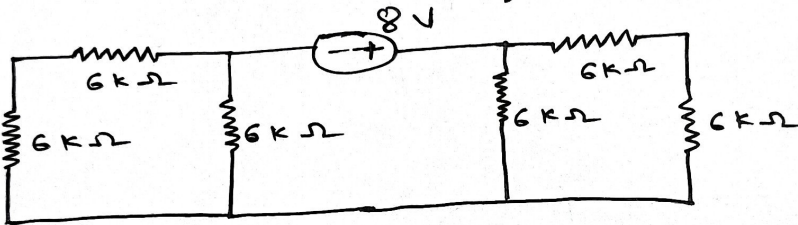ques 4: Find the current I of the circuit given below




Ans:

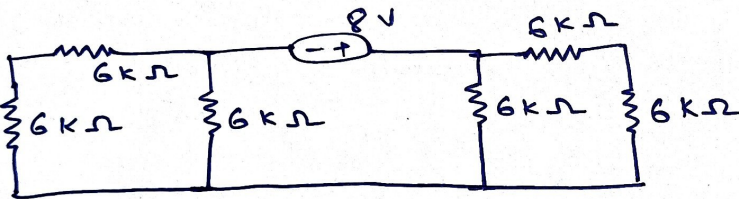


$$6 \text{ k}\Omega + 6 \text{ k}\Omega = 12 \text{ k}\Omega$$
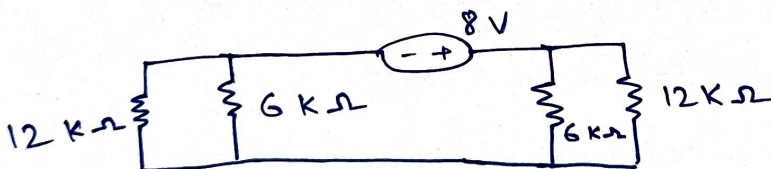
$$6 \text{ k}\Omega + 6 \text{ k}\Omega = 12 \text{ k}\Omega$$




$$R_{eq} = \frac{12 \times 6}{12 + 6} = 4 \text{ k}\Omega$$
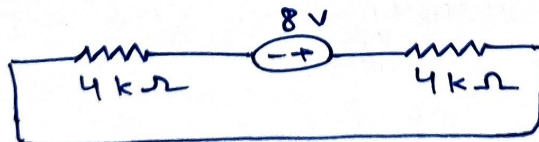
$$R_{eq} = \frac{12 \times 6}{12 + 6} = 4 \text{ k}\Omega$$




$$R_{eq} = 8 \text{ k}\Omega$$

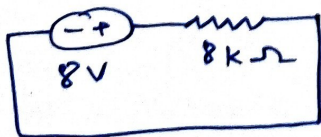

$$I = \frac{8 \text{ V}}{8 \text{ k}\Omega}$$

$$I = 1 \text{ mA}$$

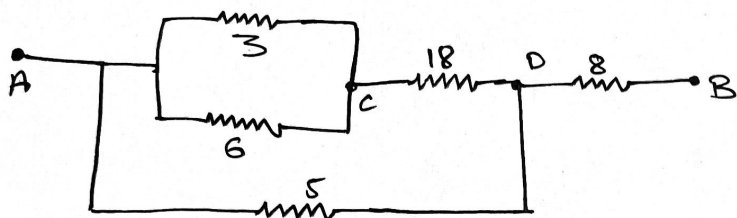Ques 5: Calculate the effective resistance of the following combination of resistances in ohm and the voltage drop across each resistance when a P.D. of 60V is applied across AB.



Ans: Resistance between AC = $6 \parallel 3 = 2 \Omega$

Resistance between ACD = $18 + 2 = 20 \Omega$

Resistance between AD = $20 \parallel 5 = 4 \Omega$

\therefore Resistance between AB = $4 + 8 = 12 \Omega$

Total current = $\frac{60}{12} = \underline{5A}$

Current through 5Ω resistance = $5 \times \frac{20}{25} = 4A$

Current in Branch ACD = $5 \times \frac{5}{25} = 1A$.


\therefore PD across 3Ω and 6Ω resistors = $1 \times 2 = 2V$

PD across 18Ω resistors = $1 \times 18 = 18V$



PD across 5Ω resistors = $4 \times 5 = 20V$

PD across 8Ω resistors = $5 \times 8 = 40V$

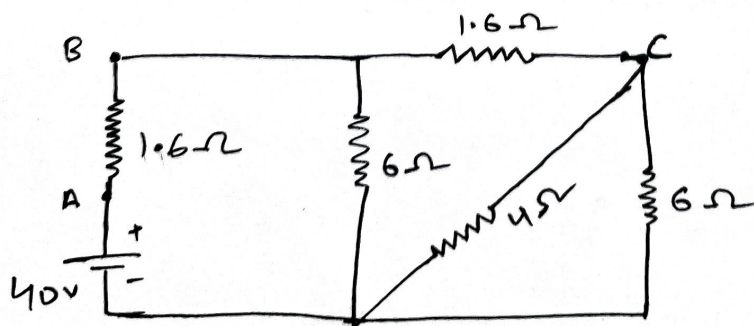Ques 6: Find current through 4Ω resistance of the circuit.



Ans :

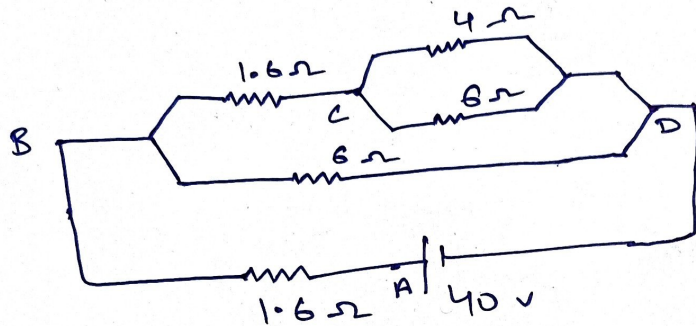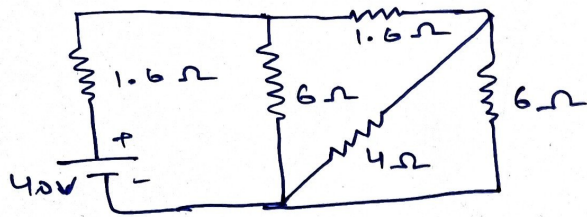

Resistance b/w C D = $4 \parallel 6 = 2.4 \Omega$

Total Resistance b/w BCD = $1.6 + 2.4 = 4 \Omega$

Total Resistance b/w BD = $4 \parallel 6 = 2.4 \Omega$

Total Resistance in the circuit = $2.4 + 1.6 = 4 \Omega$


Current = $\frac{40}{4} = 10 \text{ A}$

Current in Branch BCD = $\frac{10 \times 6}{6 + 4} = 6 \text{ A}$



Current in 4Ω resistor = $\frac{6 \times 6}{6 + 4} = 3.6 \text{ A}$

Current = 3.6 A

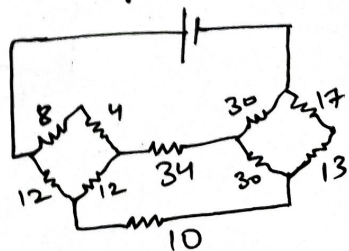Ques 7 : Calculate the current flowing through the 10Ω resistor by using any method.



Ans:

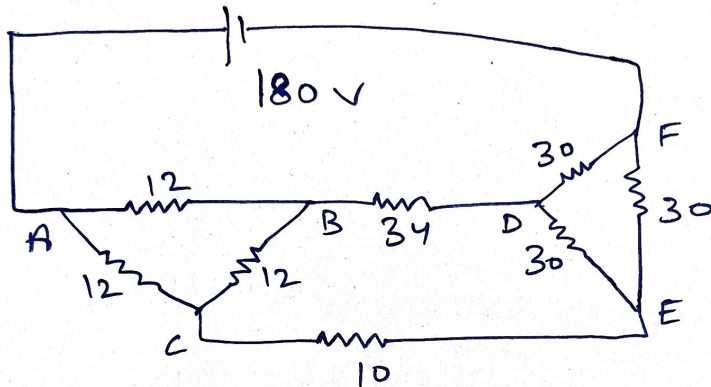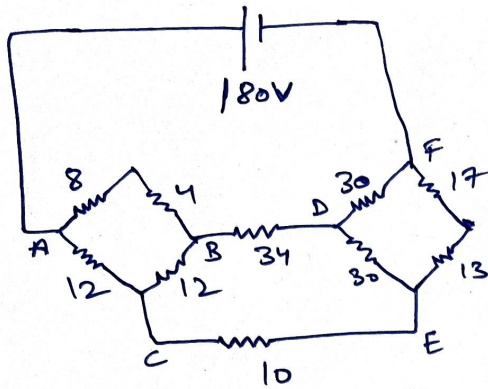

Converting Delta ABC to star

Converting Delta DEF to star

~~$$R_A = R_B = R_C = \frac{30 \times 30}{30 + 30 + 30}$$~~


$$R_D = R_E = R_F = \frac{30 \times 30}{30 + 30 + 30}$$

~~$$R_D = R_E = R_F = 10$$~~

$$R_D = R_E = R_F = 10 \Omega$$

$$R_A = R_B = R_C = \frac{12 \times 12}{12 + 12 + 12}$$

$$R_A = R_B = R_C = 4 \Omega$$

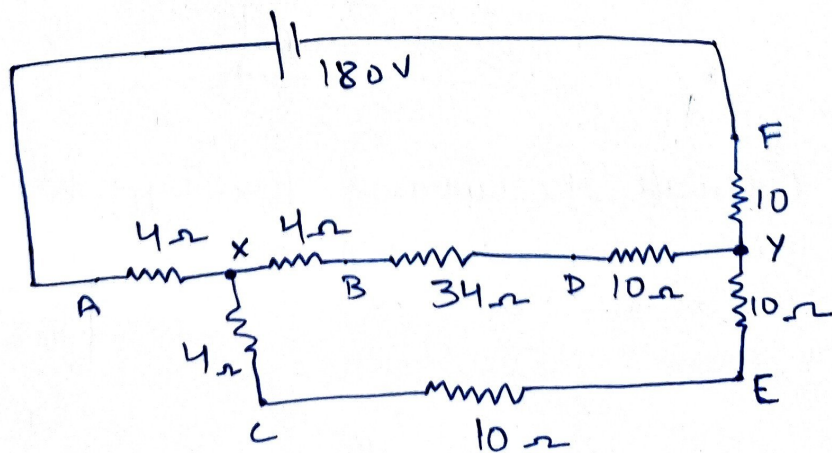

$$\text{Resistance b/w XBDY} = 4 + 3 + 4 + 10 = 48 \Omega$$

$$\text{Resistance b/w XCEY} = 4 + 10 + 10 = 24 \Omega$$

$$\text{Resistance b/w XY} = 48 \parallel 24 = 16 \Omega$$

$$\text{Total Resistance b/w AF} = 4 + 16 + 10 = 30 \Omega$$


$$\text{Current} = \frac{180}{30} = 6 \text{ A}$$

$$\boxed{I = 6 \text{ A}}$$

$$\text{Current in Branch XCEY} = \frac{6 \times 48}{48 + 24} = 4 \text{ A}$$

$$\boxed{\text{Current in } 10 \Omega \text{ Resistor} = 4 \text{ A}}$$

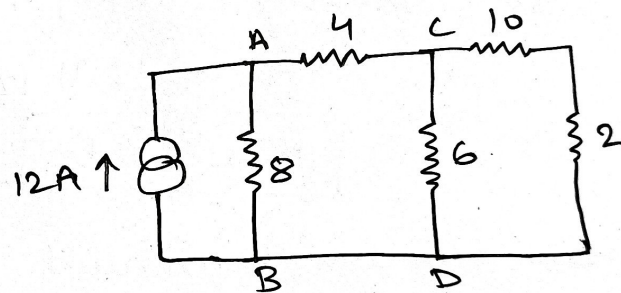Ques 8: Using Norton's Theorem calculate current in the 6Ω resistor




Ans: Using Norton's Theorem

Step 1: Identify Load Resistor

$$\boxed{R_L = 6 \Omega}$$

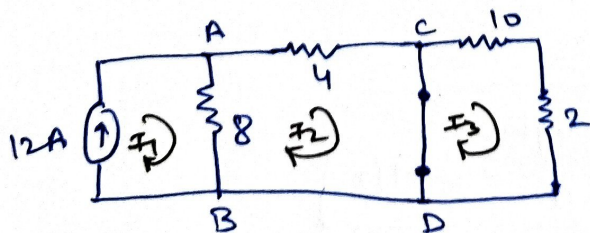Step 2: Replace R_L with short circuit branch and calculate I_N



→ I_3 was short circuited so, $\boxed{I_3 = 0}$

Applying KVL in Mesh ①

$$12A = I_1$$

Applying KVL in Mesh ②

$$-8[I_2 - I_1] - 4I_2 = 0$$


$$-12I_2 + 8I_1 = 0$$

$$-12I_2 = -86A$$

$$I_2 = 8A$$

$$I_N = I_2 = 8A$$

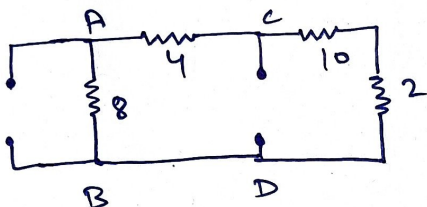Step 3: Remove R_L and replace all active sources with their internal resistances. Calculate R_N




$$\text{Total Resistance} = (8+4) \parallel (10+2)$$

$$= 12 \parallel 12$$

$$R_N = 6 \Omega$$

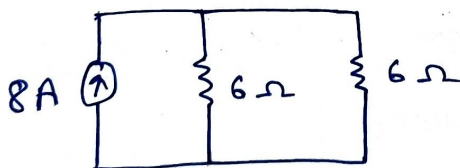Step 4: Draw Norton's equivalent circuit and calculate I_L



$$I_L = \frac{8 \times 6}{6+6}$$

$$I_L = 4A$$


$$\text{Current through } 6 \Omega \text{ Resistance} = 4A$$

Ques 9: state Thevenin's Theorem and Norton's Theorem and verify it by Illustration.

ans: Thevenin Theorem: According to Thevenin's Theorem, any linear network irrespective of its complexity can be reduced into a thevenin equivalent circuit having thevenin voltage or open circuit voltage $[V_{th}]$, thevenin / Equivalent Total Resistance $[R_{th}]$ with load resistance $[R_L]$ connected in series with $[R_{th}]$.

Norton's Theorem: According to Norton's Theorem, any linear electric network irrespective of its complexities can be reduced into a Norton's Equivalent circuit having a Norton's short circuit current in parallel with Norton's equivalent resistance R_N with parallel load resistor R_L .

Illustration:

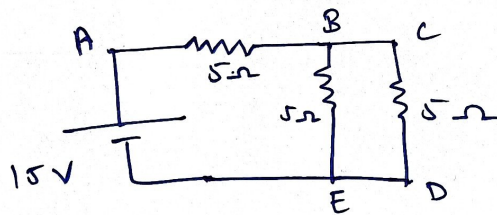

using Ohm's law:

$$R_{eq} = 5 + 5 \parallel 5$$

$$= 5 + 2.5$$

$$R_{eq} = 7.5 \Omega$$

$$I = \frac{15}{7.5} = 2$$

$$I = 2A$$

$$\text{Current in Branch BE} = \frac{2 \times 5}{5+5} = 1$$

$$\text{current in BE} = 1A$$

Thevenin

step 1: Identify load resistance


$$R_L = 5 \Omega$$

Illustration
Norton

step 1: Identify load resistance

$$R_L = 5 \Omega$$

Step 2: Remove R_L and calculate V_{Th}

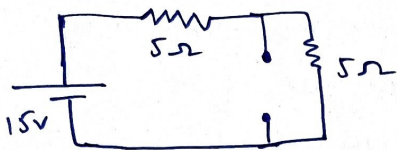


$$I = \frac{15}{10} = 1.5A$$

$$V_{Th} = 5 \times 1.5$$

$$V_{Th} = 7.5V$$

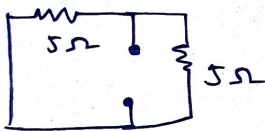
Step 3: Remove R_L and replace all active sources with their internal resistances.



$$R_{Th} = \frac{5 \times 5}{5 + 5}$$


$$R_{Th} = 2.5\Omega$$

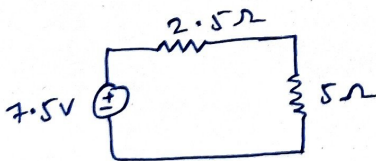Step 4: Draw Thevenin's equivalent circuit



$$I = 1A$$

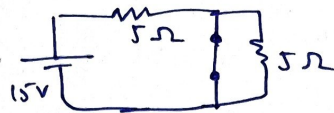
Step 2: Replace R_L with short circuit branch and calculate I_N



$$I = \frac{15}{5} = 3A$$

$$I_N = 3A$$

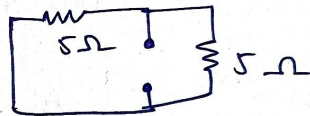
Step 3: Remove R_L and replace all active sources with their internal resistances



$$R_N = \frac{5 \times 5}{5 + 5}$$

$$R_N = 2.5\Omega$$

Step 4: Draw Norton's equivalent circuit

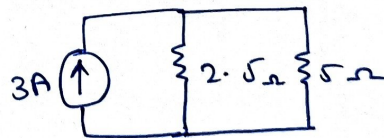


$$I = 1A$$


As all the three calculated values are same. Hence, verified.

Ques 10: Give the derivation for star to Delta and Delta to Star transformation.

Ans: Delta to Star Transformation

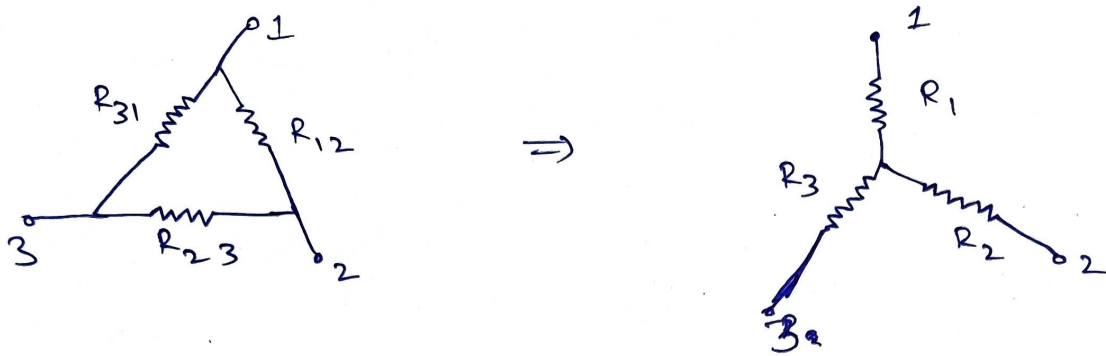

Equivalent circuit between ① & ②

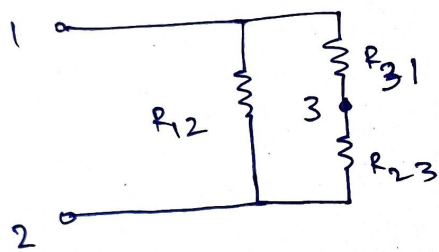


$$R_{eq} = R_{12} \parallel (R_{31} + R_{23})$$

$$R_{eq})_{12} = \frac{R_{12} (R_{31} + R_{23})}{R_{12} + R_{31} + R_{23}}$$

Similarly,

$$R_{eq})_{23} = \frac{R_{23} (R_{12} + R_{31})}{R_{12} + R_{23} + R_{31}}$$
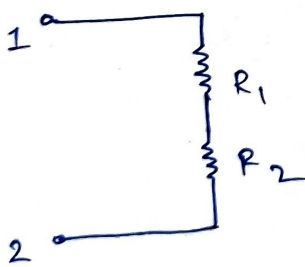
$$R_{eq})_{31} = \frac{R_{31} (R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}}$$



$$R_{eq})_{12} = R_1 + R_2$$

Similarly,

$$R_{eq})_{23} = R_2 + R_3$$

$$R_{eq})_{31} = R_3 + R_1$$

$$R_1 + R_2 = \frac{R_{12} (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (i)}$$

$$R_2 + R_3 = \frac{R_{23} (R_{31} + R_{12})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (ii)}$$

$$R_3 + R_1 = \frac{R_{31} (R_{23} + R_{12})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (iii)}$$

$$\textcircled{1} - \textcircled{11} \Rightarrow R_1 - R_3 = \frac{R_{12} \cdot R_{23} + R_{12} \cdot R_{31} - R_{23} \cdot R_{31} - R_{23} \cdot R_{12}}{R_{12} + R_{23} + R_{31}}$$

$$R_1 - R_3 = \frac{R_{12} \cdot R_{31} - R_{23} \cdot R_{31}}{R_{12} + R_{23} + R_{31}} \quad \text{--- } \textcircled{14}$$

$\textcircled{14} + \textcircled{11}$,

$$2R_1 = \frac{R_{12} \cdot R_{31} - R_{23} \cdot R_{31} + R_{31} \cdot R_{12} + R_{31} \cdot R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$2R_1 = \frac{2R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$


$$R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$

Similarly,


$$R_2 = \frac{R_{23} \cdot R_{12}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{31} \cdot R_{23}}{R_{12} + R_{23} + R_{31}}$$

Star to Delta Transformation

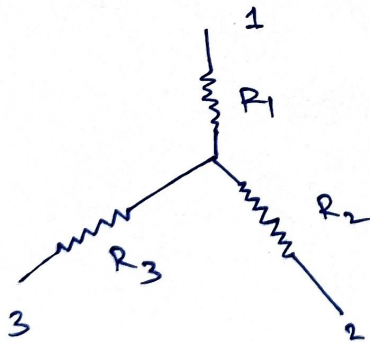

\Rightarrow

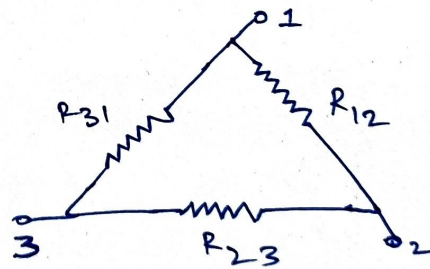

$$R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}} \quad \text{--- } \textcircled{1}$$

$$R_2 = \frac{R_{23} \cdot R_{12}}{R_{12} + R_{23} + R_{31}} \quad \text{--- } \textcircled{11}$$

$$R_3 = \frac{R_{31} \cdot R_{23}}{R_{12} + R_{23} + R_{31}} \quad \text{--- } \textcircled{111}$$

$$R_1 \cdot R_2 = \frac{(R_{12} \cdot R_{31})(R_{23} \cdot R_{12})}{(R_{12} + R_{23} + R_{31})^2} = \frac{R_{12}^2 \cdot R_{23} \cdot R_{31}}{(R_{12} + R_{23} + R_{31})^2} \quad \text{--- (4)}$$

$$R_2 \cdot R_3 = \frac{R_{23}^2 \cdot R_{12} \cdot R_{31}}{(R_{12} + R_{23} + R_{31})^2} \quad \text{--- (5)}$$

$$R_3 \cdot R_1 = \frac{R_{31}^2 \cdot R_{12} \cdot R_{23}}{(R_{12} + R_{23} + R_{31})^2} \quad \text{--- (6)}$$

$$(4) + (5) + (6)$$

$$R_1 \cdot R_2 + R_2 \cdot R_3 + R_3 \cdot R_1 = \frac{R_{12} \cdot R_{23} \cdot R_{31} (R_{12} + R_{23} + R_{31})}{(R_{12} + R_{23} + R_{31})^2}$$

$$R_1 \cdot R_2 + R_2 \cdot R_3 + R_3 \cdot R_1 = \frac{R_{12} \cdot R_{23} \cdot R_{31}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (7)}$$

using (7) & (1)

$$R_1 \cdot R_2 + R_2 \cdot R_3 + R_3 \cdot R_1 = R_1 \cdot R_{23}$$

$$R_{23} = \frac{R_1 \cdot R_2 + R_2 \cdot R_3 + R_3 \cdot R_1}{R_1}$$

Similarly,

$$R_{31} = \frac{R_1 \cdot R_2 + R_2 \cdot R_3 + R_3 \cdot R_1}{R_2}$$

$$R_{12} = \frac{R_1 \cdot R_2 + R_2 \cdot R_3 + R_3 \cdot R_1}{R_3}$$